

Pulse Detector for specific frequencies in Verilog

Aristotle University of Thessaloniki (AUTH)

Course: Digital Systems

Mastoreka Maria

19/06/2025



ΤΜΗΜΑ ΦΥΣΙΚΗΣ Α.Π.Θ.
Πρόγραμμα Μεταπτυχιακών Σπουδών
Ηλεκτρονικής Φυσικής
(Ραδιοηλεκτρολογίας)



Project goal

- Detect the frequency of an incoming digital signal
- Valid frequency values: *10 MHz, or 20 MHz, 50 MHz.*

Challenges

- Digital circuits cannot directly detect frequency — they react to pulses
- The input signal is asynchronous to the system clock. → Without synchronization, metastability may occur

We must:

1. Detect the time between rising edges (period)
2. Classify the signal based on this period




System Architecture & Approach

- ✓ Synchronize the input and avoid metastability
- ✓ Detect rising edges ($0 \rightarrow 1$ transitions)
- ✓ Measure the time between edges (signal period)
- ✓ Classify the period into a frequency range (50 MHz, 10 MHz, 20 MHz)
- ✓ Activate the corresponding output signal

Modules

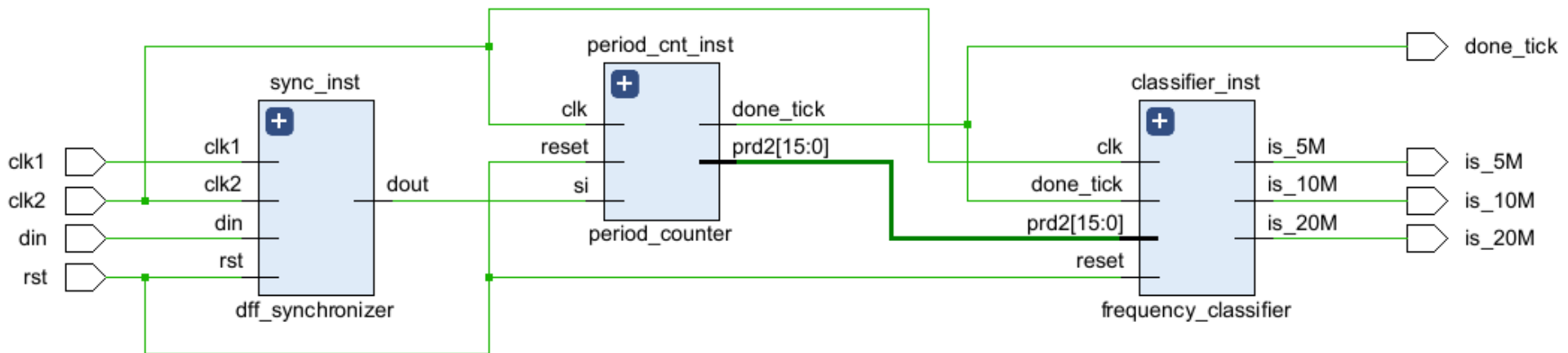1. Dual Flip Flop Synchronizer
2. Period counter
3. Frequency Classifier



Dff Synchronizer



Flip-flops require proper timing: setup time (t_{su}) and hold time (t_h). If these constraints are violated, metastability may occur.

Metastability

- Occurs when the input of a flip-flop changes very close to a clock edge
- The output may become unstable or undefined
- A common issue with asynchronous signals from external sources

Solution : Dual Flip-Flop Synchronizer

 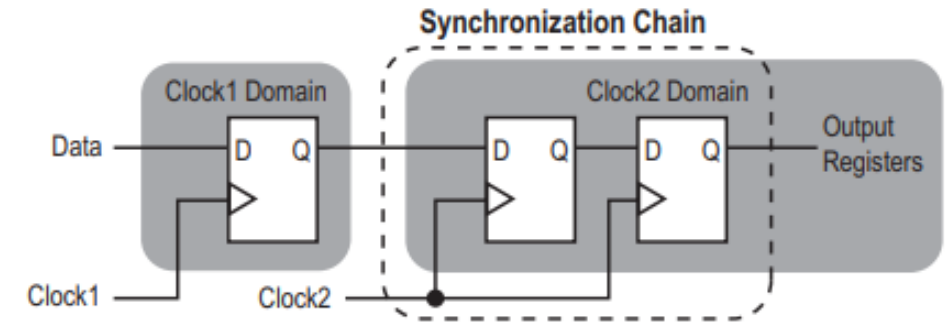- The first flip-flop captures the asynchronous input
- The second delays the signal by one clock cycle, allowing it to stabilize. This reduces the probability of metastability errors
- The more flip-flops added, the lower the error probability, but also the longer the delay
- In this design: transition from slower ($clk1$) to faster clock ($clk2$)



```
// Module Name: dff_synchronizer
module dff_synchronizer(
    input wire clk1,
    input wire clk2,
    input wire rst,
    input wire din,
    output wire dout
);
    reg din_flop;
    (* ASYNC_REG = "TRUE" *) reg dmeta;
    (* ASYNC_REG = "TRUE" *) reg dmeta2;

    always @(posedge clk1 or posedge rst) begin
        if (rst) din_flop <= 1'b0;
        else    din_flop <= din; end

    always @(posedge clk2 or posedge rst) begin
        if (rst) begin
            dmeta <= 1'b0;
            dmeta2 <= 1'b0;
        end else begin
            dmeta <= din_flop;
            dmeta2 <= dmeta;
        end
        end
    assign dout=dmeta2;
endmodule
```




Period Counter

This module measures the period of the input pulse signal.

Key Features

 1. Rising Edge Detection using delay registers (delay_reg, si_d1) and comparison logic
2. Implemented as a 3-state FSM, since delay_reg represents si delayed by 2 clock cycles
 - ✓ Rising edge is detected by identifying the 110 sequence in the delayed signal
3. The internal counter increments on every clock cycle, measuring the time between two rising edges
4. The measured period is stored in prd2
5. Done_tick is activated when a new measurement is available



```
assign edge1 = ~delay_reg & si;

always @(posedge clk or posedge reset) begin
    if (reset) begin
        state_reg <= A;
        period_reg <= 16'd0;
        period_prev <= 16'd0;
        prd2 <= 16'd0;
        si_d1 <= 1'b0;
        delay_reg <= 1'b0;
    end else begin
        state_reg <= state_next;
        period_prev <= period_reg;
        prd2 <= period_prev;
        si_d1 <= si;
        delay_reg <= si_d1;

        if (state_reg == A || state_reg == C)
            period_reg <= period_reg + 1;
        else if (state_reg == B)
            period_reg <= 16'd0;
    end
end

always @(*) begin
    done_tick = 1'b0;
    case (state_reg)
        A: if (edge1) begin
            state_next = B;
            done_tick = 1'b1;
        end else state_next = A;
        B: if (edge1)
            state_next = C;
        else
            state_next = A;
        C: state_next = A;
        default: state_next = A;
    endcase
end
```



Frequency Classifier

This module classifies the signal frequency based on the period measured by the period_counter.

Key Features:

- The period value (prd) is used to estimate the input frequency
- Once done_tick is activated, it checks if the measured period corresponds to one of the predefined frequency ranges
- The signal is classified into 10 MHz, or 20 MHz, 50 MHz.
- The corresponding output flag is asserted (is_20M, is_10M, is_50M)

Example Calculation:

$$\text{Prd} = \frac{T_{\text{signal}}}{T_{\text{clock}}} \quad \text{For 50 MHz} \rightarrow \text{prd} = \frac{50\text{ns}}{5\text{ns}} = 10$$

```
always @(posedge clk or posedge reset) begin
    if (reset) begin
        is_10M <= 0;
        is_20M <= 0;
        is_5M <= 0;

    end else begin
        // Default:
        is_5M <= 0;
        is_10M <= 0;
        is_20M <= 0;

        if (done_tick) begin

            if (prd2 == 16'd16)
                is_10M <= 1'b1;
            else if (prd2 == 16'd6)
                is_20M <= 1'b1;
            else if (prd2 == 16'd36)
                is_5M <= 1'b1;


        end
    end
end
```



Simulation (1/3)


10 MHz Input Signal

 - The classifier correctly identifies the signal as 10 MHz and activates the is_10M output flag
- The result confirms correct detection and classification logic




Simulation (2/3)

20 MHz Input Signal

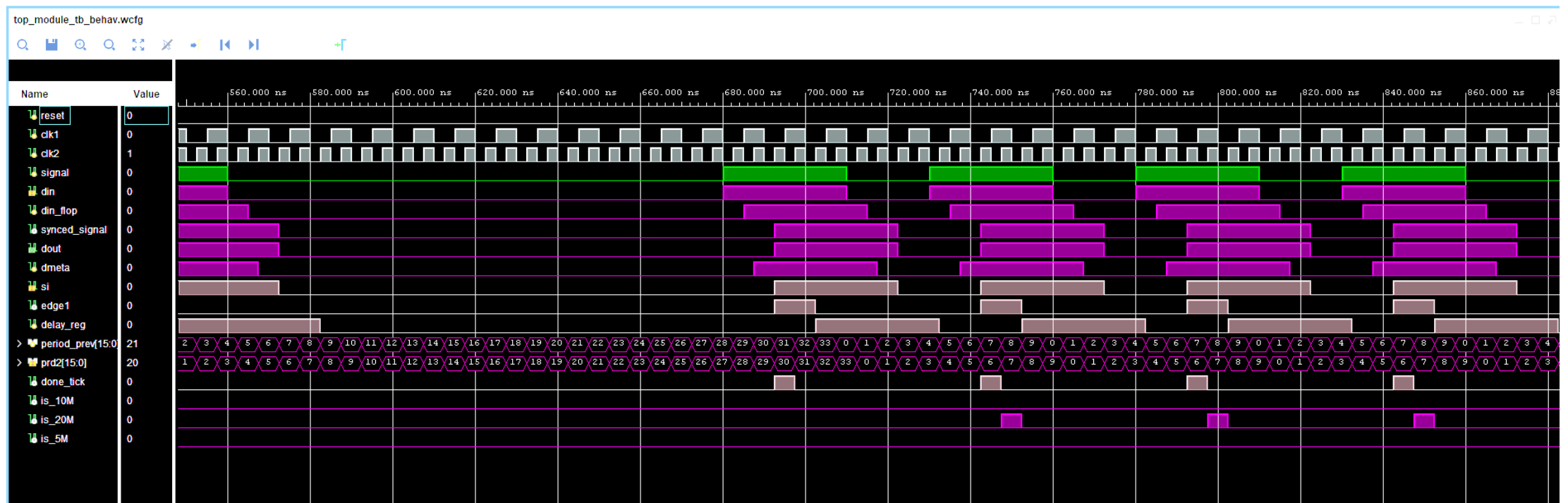


Simulation (3/3)

50 MHz Input Signal

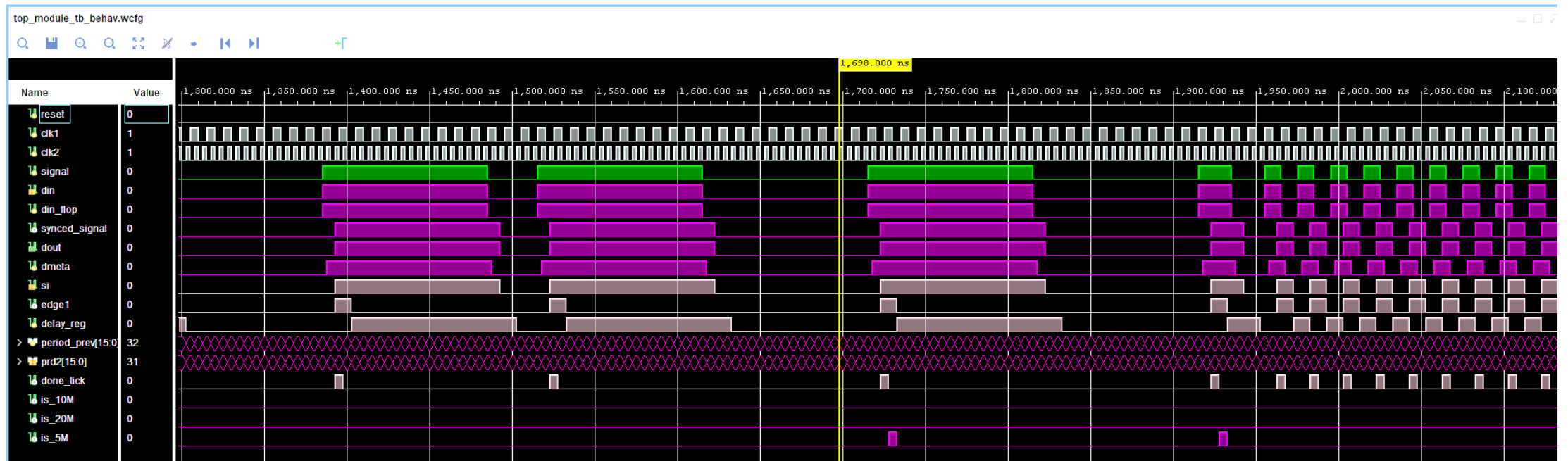

Synthesis and Implementation

Schematic

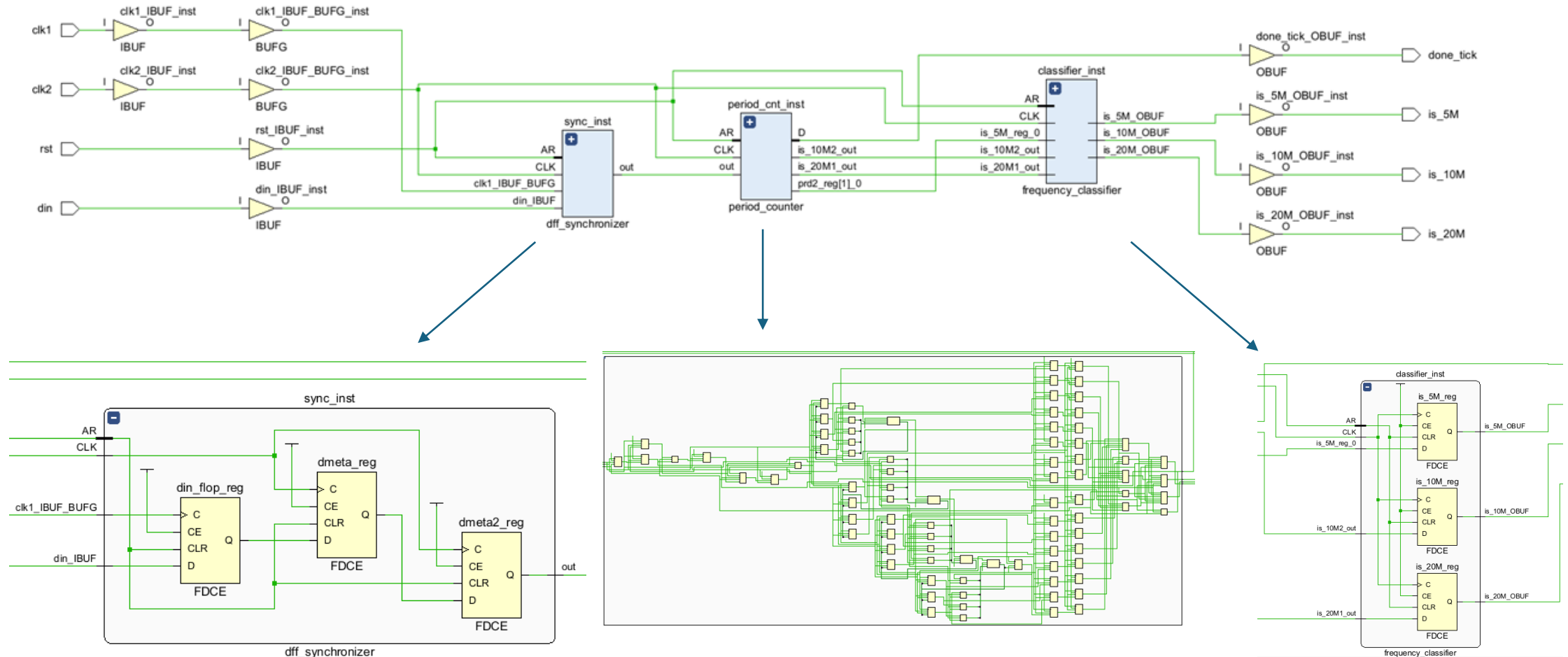

Results




Timing Results

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 2.188 ns	Worst Hold Slack (WHS): 0.119 ns	Worst Pulse Width Slack (WPWS): 2.000 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 73	Total Number of Endpoints: 73	Total Number of Endpoints: 61

 All user specified timing constraints are met.



Resource Utilization

Name	Slice LUTs (20800)	Slice Registers (41600)	Slice (8150)	LUT as Logic (20800)	Bonded IOB (106)	BUFGCTRL (32)
top_module	26	59	13	26	8	2
classifier_inst (frequency_classifier)	0	3	2	0	0	0
period_cnt_inst (period_counter)	26	53	12	26	0	0
sync_inst (dff_synchronizer)	0	3	2	0	0	0




Power Consumption





Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.072 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 25.4°C
Thermal Margin: 59.6°C (11.9 W)
Effective θ_{JA} : 5.0°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Medium

On-Chip Power

 

Package and Device View

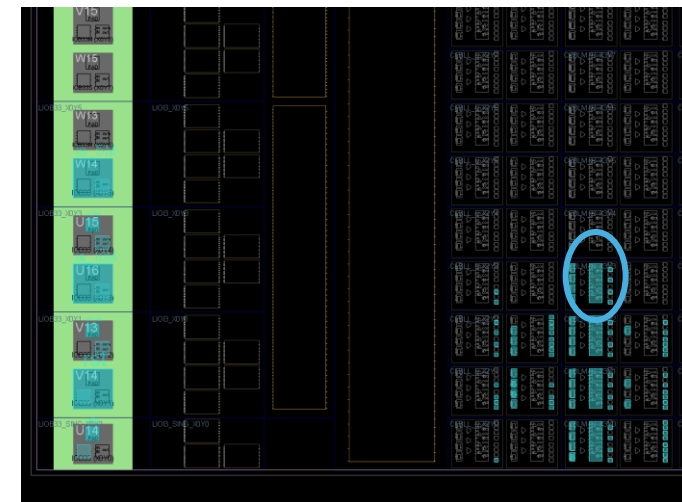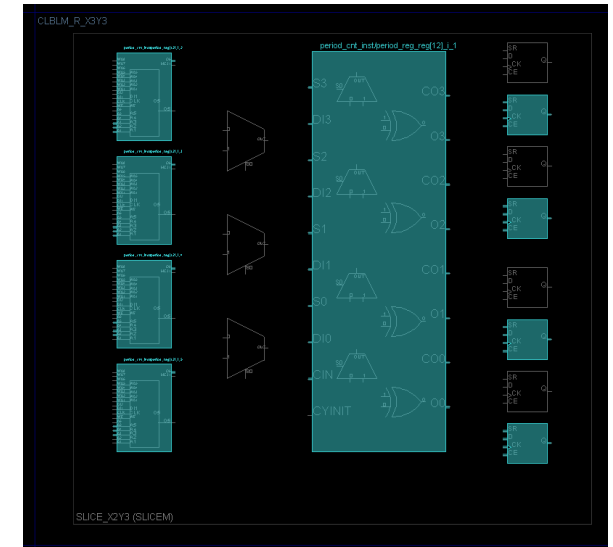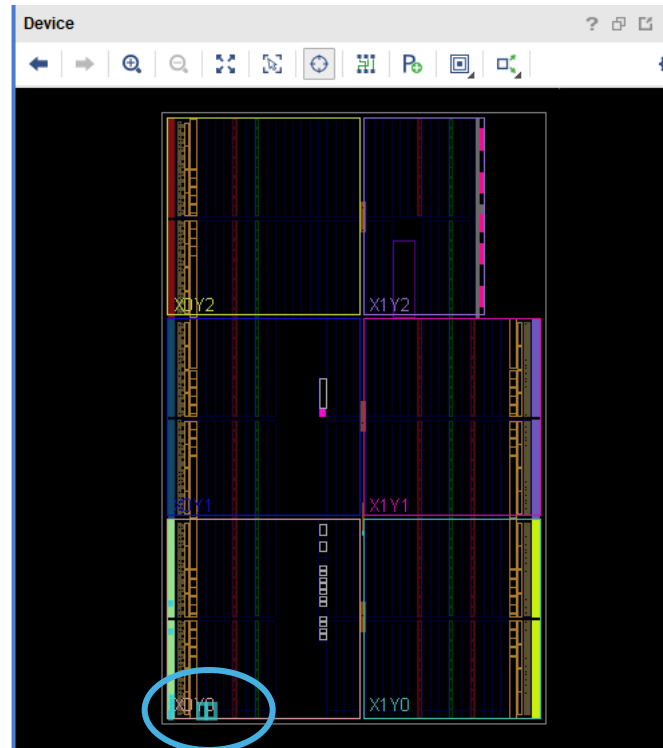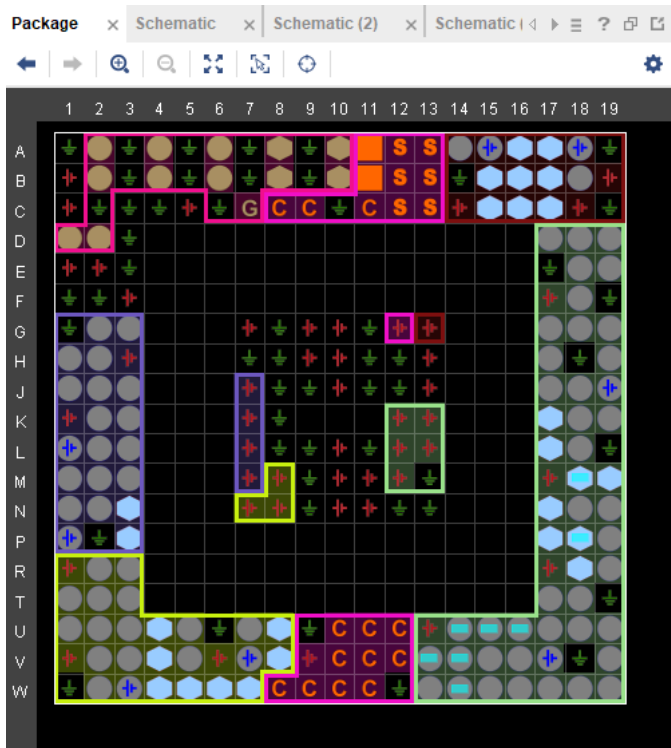

Thank you!

